


Topics for Today:


- Announcements
- Matlab - now we are ready to begin using it.
- Office hrs: 2:05-2:55pm M,W,F
- Office: EERC 614. Phone: 906.487.2857
- Recommended problems from Ch.3, solutions posted
- Next: Transmission Line Parameters, Chapters 4,5,6

Transformers - wrapup on off-nominal turns ratio 

Synchronous Machines - Chapter 3.


- Basic internal structure of machines, cylindrical vs. salient
 - Field windings
 - Calculation with X_d and X_q .
 - Calculation Example(s)
 - Concepts behind SYNCH exercise set.
 - S-S behavior - X_d ; Dynamic behavior - X_d'
 - Short-circuit behavior - X_d'' ; s-s, transient, subtransient
- 

$\vec{y}_1 =$

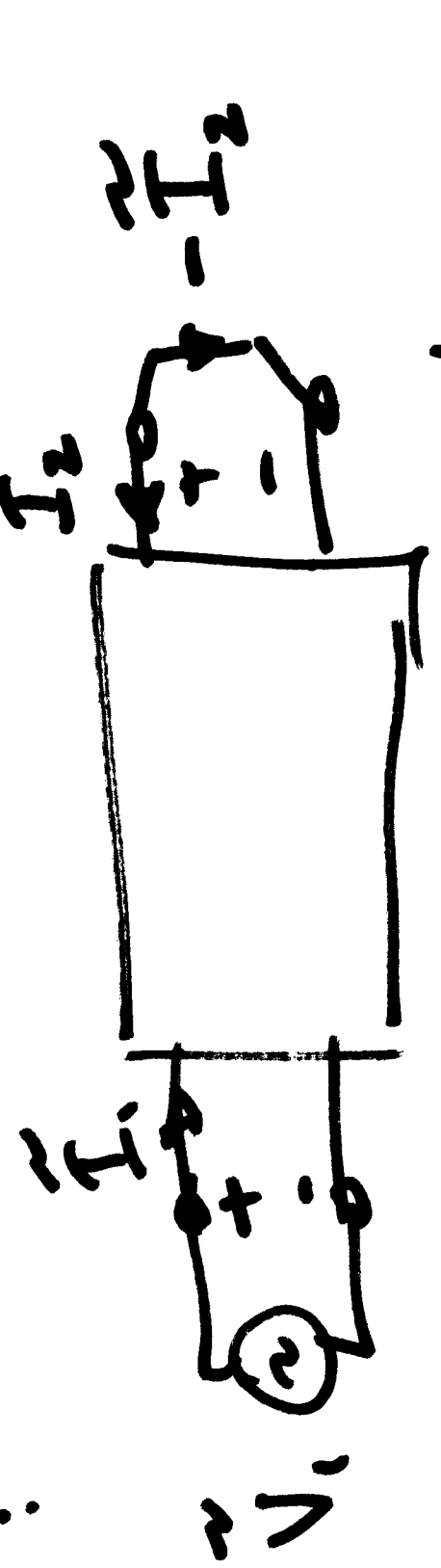



$$\vec{y}_1 = \begin{matrix} I_1 \\ I_2 \end{matrix} \bigg| \begin{matrix} V_2 = 0 \end{matrix}$$

$$\vec{y}_2 = \begin{matrix} I_2 \\ I_1 \end{matrix} \bigg| \begin{matrix} V_1 = 0 \end{matrix}$$

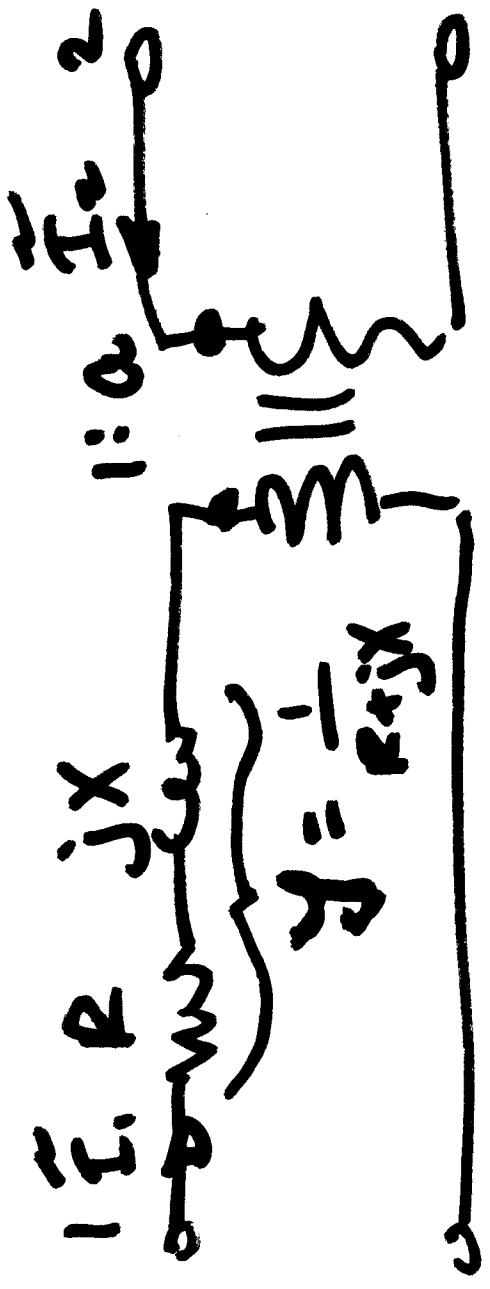
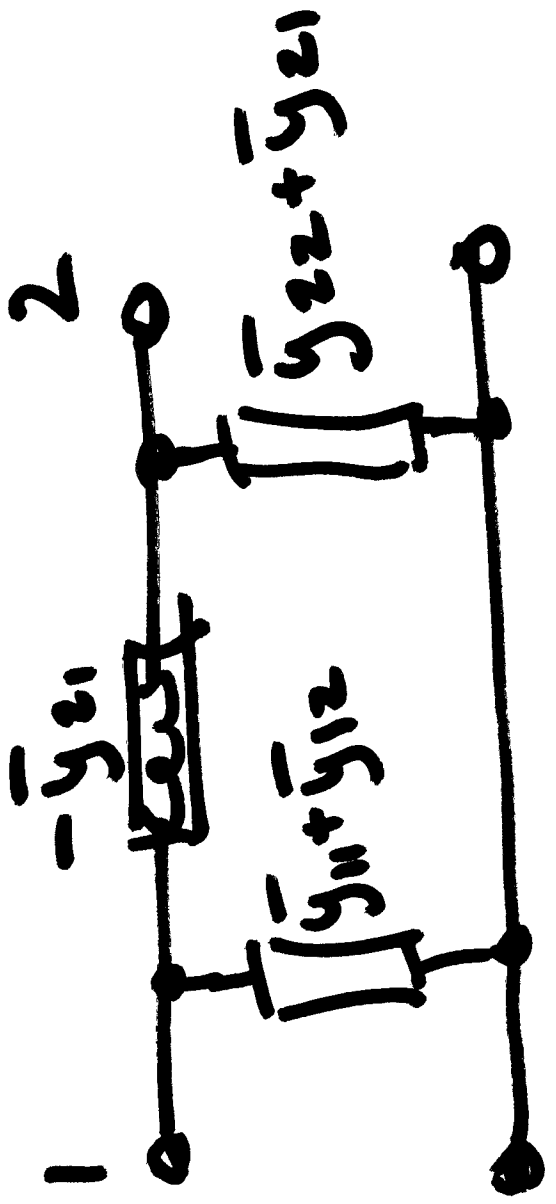
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} H_{11} & H_{12} \\ H_{21} & H_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



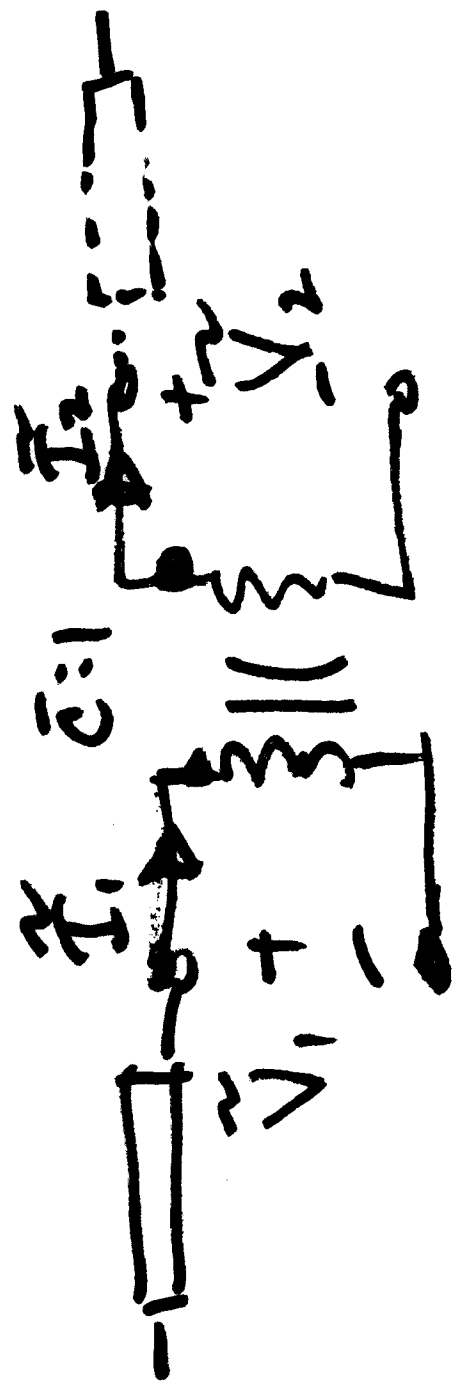

$$Z = jX$$


$$\vec{S}_1 = \vec{S}_2 \rightarrow$$

$$V_1 I_1^* = V_2 I_2^*$$

$$\frac{I_2^*}{I_1^*} = \frac{V_1}{V_2} = \bar{c}$$

$$\frac{I_2^*}{I_1^*} = \bar{c}$$

Ex: 13


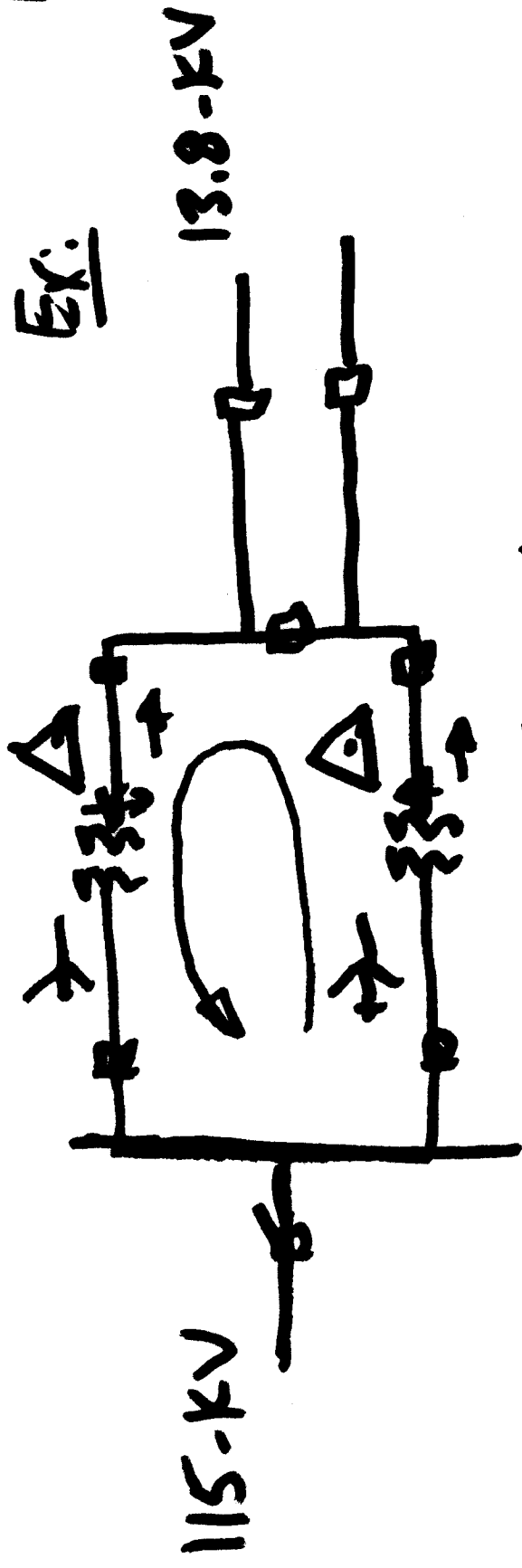


Circulating vars

Energization Testing of Var Meters

Detailed derivations!

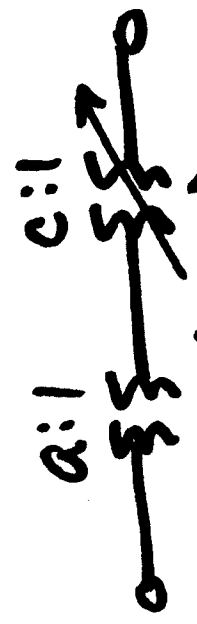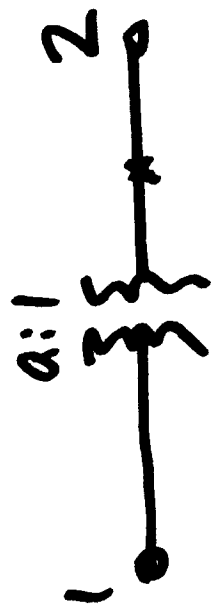Basis Approach: Develop π -Equiv and handle just like T-Line.



Top-Changers

- LTC's
- Phase-Shift

NOMINAL TRANS RATIO \uparrow \pm Adjustment (PS) in phase angle (LTC) or volt mag (LTC)

XFMRs - Use Φ L-N ($\Phi A-N$)
 per phase Eguin.



Modify
 $y_{55} - y_{56}$
 $y_{65} - y_{66}$

In [Ybus] $y_{56} = -\frac{1}{Z_{66}}$

(and y_{65})
 $y_{55} = y_{55} + Z_{54}$
 $y_{66} = y_{66} + "$

Basis 2-winding
 XFMR is simple.

How about?
 - LTC (or TCUL)
 - Phase Shifter (PS)

Tap Changing XFMRs - Variations (P.u. Representations)


"From" Bus "To" Bus

$$y_{sc} = \frac{1}{R+jX}$$


"C" is off-nominal turns ratio. In general C is complex.

C is real for LTC.
C is complex for PS.

If $|C| \neq 1$ then magnitude change.
If C is complex, Phase Shift.

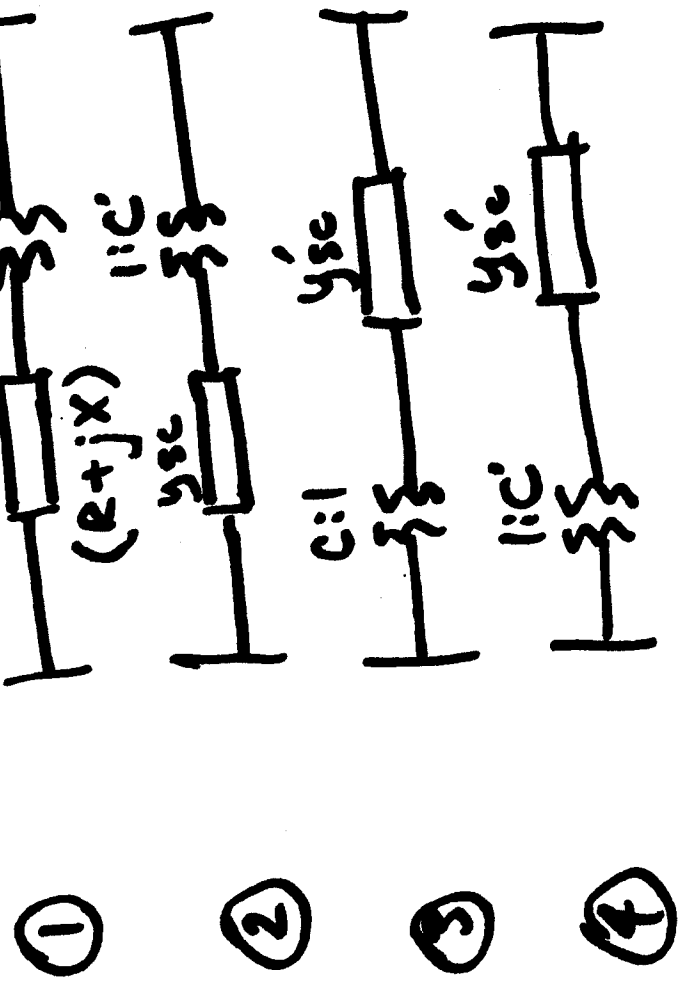


Standard Approach:

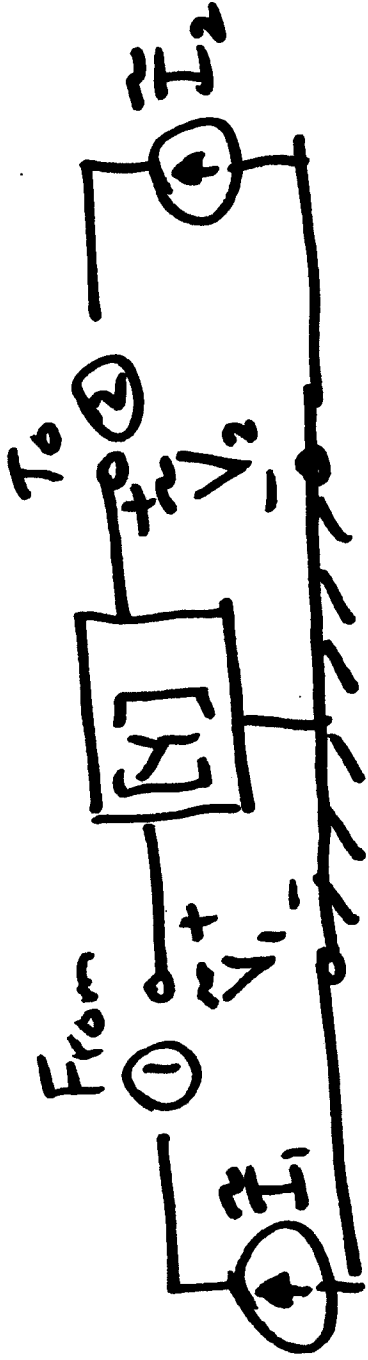

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$
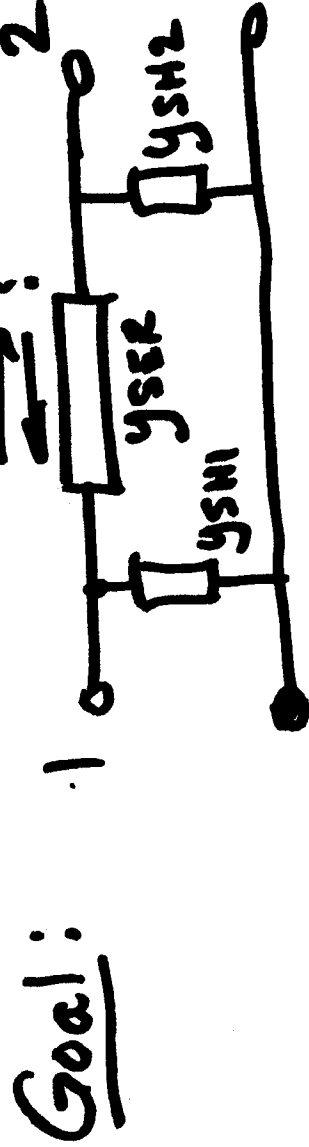
$$\begin{aligned} y_{11} &= y_{SER} + y_{SH1} \\ y_{12} &= -y_{SER} \\ y_{21} &= -y_{SER} \\ y_{22} &= y_{SER} + y_{SH2} \end{aligned}$$




TAP-CHANGERS

a

On One-Line Diags:




Conceptually:

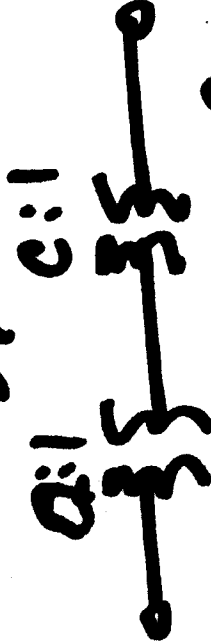


Nominal
Voltage
Ratio

↑ off-nominal
turns ratio
due to
Tap changer

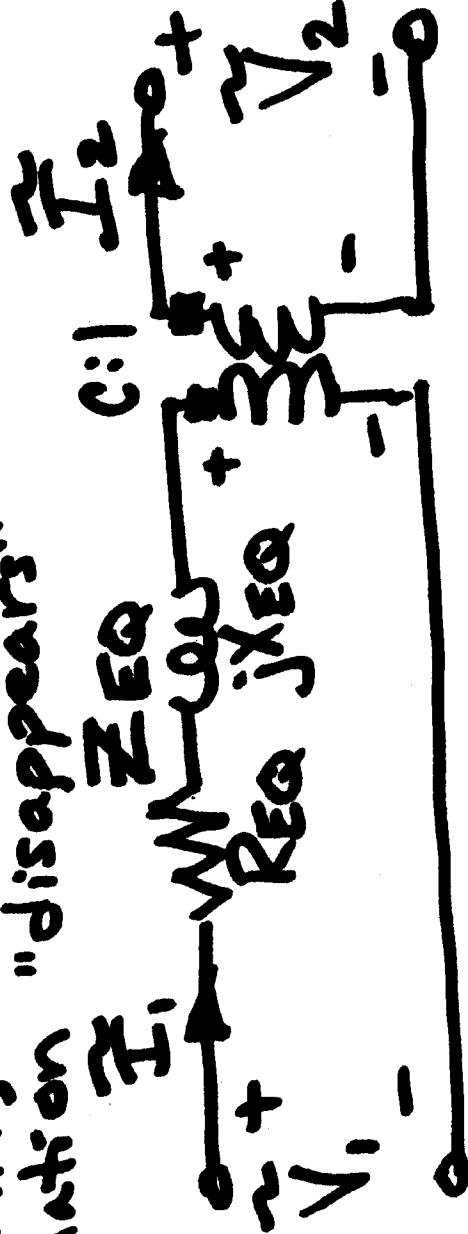In per unit, nominal
transformation "disappears"



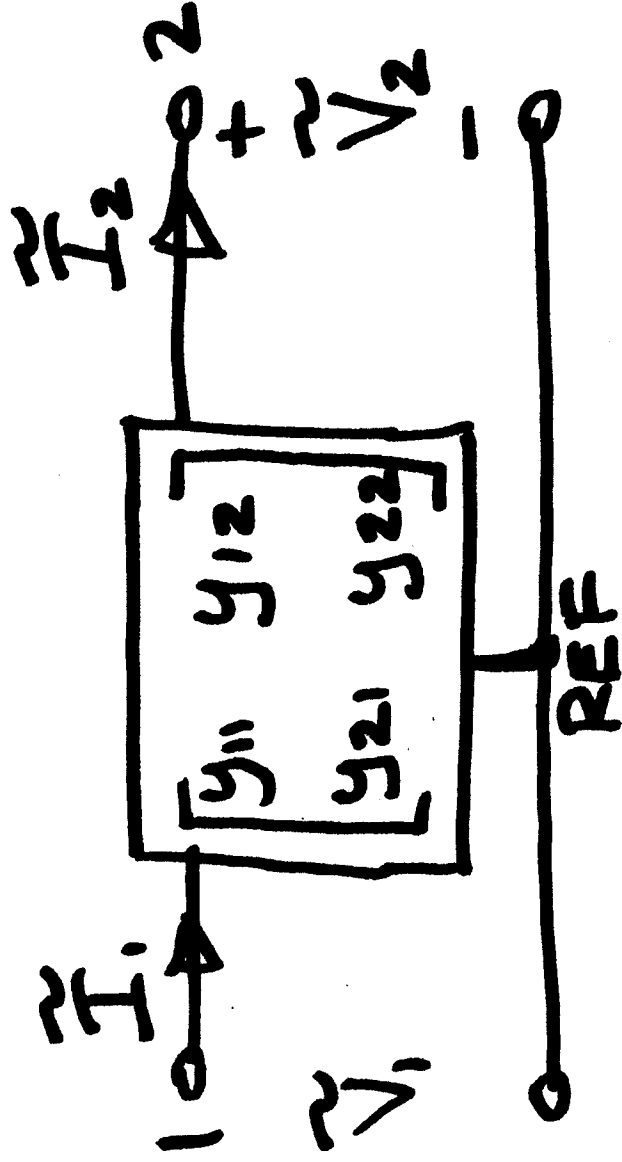
Generically, we can describe this as a 2-node [Y]



where


$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ -I_2 \end{bmatrix}$$

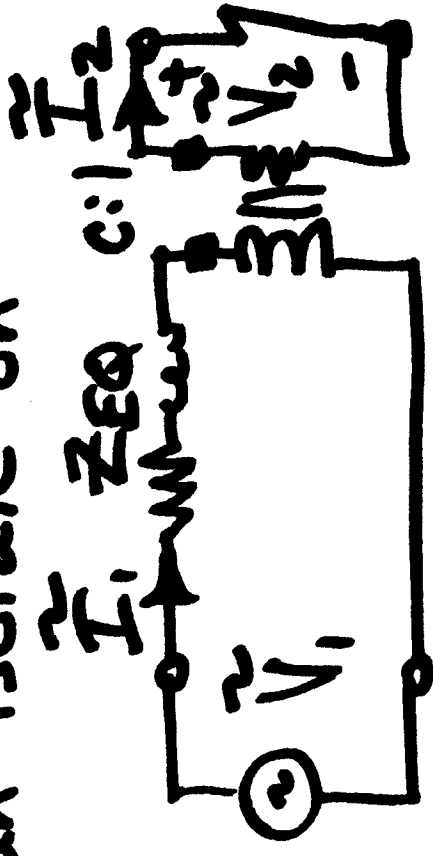Strategically using shorts ~~on~~
~~the values of [Y]~~, we can isolate on
 the values of [Y].



$$y_{11} = \frac{\tilde{I}_1}{\tilde{V}_1} \Big|_{\tilde{V}_2=0}$$
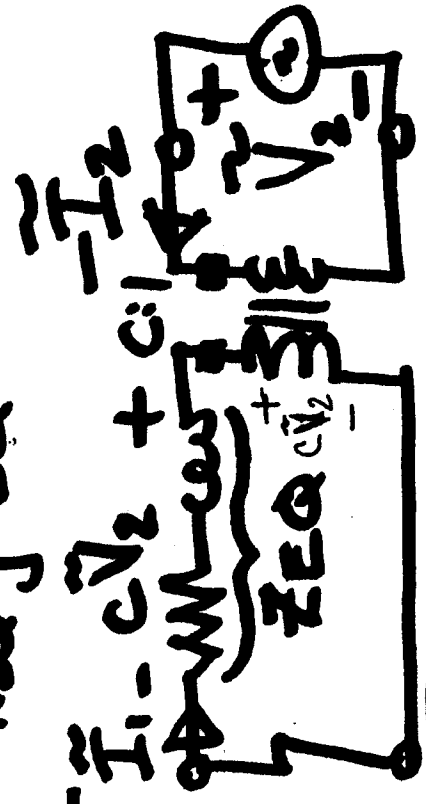
$$= \frac{1}{Z_{EQ}} = Y_{EQ} = \frac{1}{R_{EQ} + jX_{EQ}}$$



$$y_{22} = \frac{-\tilde{I}_2}{\tilde{V}_2} \Big|_{\tilde{V}_1=0}$$

$$= \frac{1}{Z_{EQ} / |C|^2} = |C|^2 Y_{EQ}$$

$$\vec{I}_1 = -\frac{c\vec{V}_2}{z_{EQ}}; \quad -\vec{I}_2 = -\frac{\vec{I}_1 \cdot c^*}{z_{EQ}} = -\left[\frac{c\vec{V}_2}{z_{EQ}}\right] c^*$$


$$= \frac{|c|^2 \vec{V}_2}{z_{EQ}}$$

Note: $\frac{I_2}{I_1} = c^*$

$$y_{12} = \frac{\tilde{I}_1}{\tilde{V}_2} \Big|_{\tilde{V}_1=0} = \frac{-C\tilde{V}_2/Z_{EQ}}{\tilde{V}_2} = -C\gamma_{EQ}^d$$

$$y_{21} = -\frac{\tilde{I}_2}{\tilde{V}_1} \Big|_{\tilde{V}_2=0} = \frac{-C^*\tilde{I}_1}{\tilde{V}_1} = -C^*\gamma_{EQ}$$

Note: Ideal XFR, by definition, has

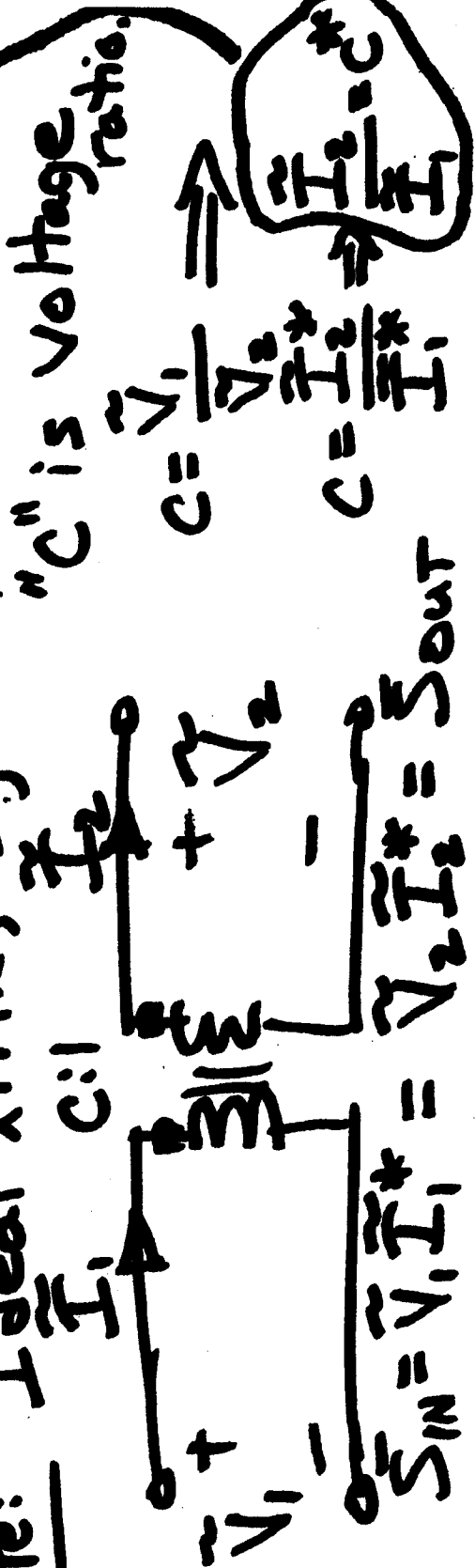


"C" is voltage ratio.

$$C = \frac{\tilde{V}_2}{\tilde{V}_1} = \frac{\tilde{I}_1}{\tilde{I}_2} = \frac{C^*}{1}$$

If we "reverse engineer" our e)

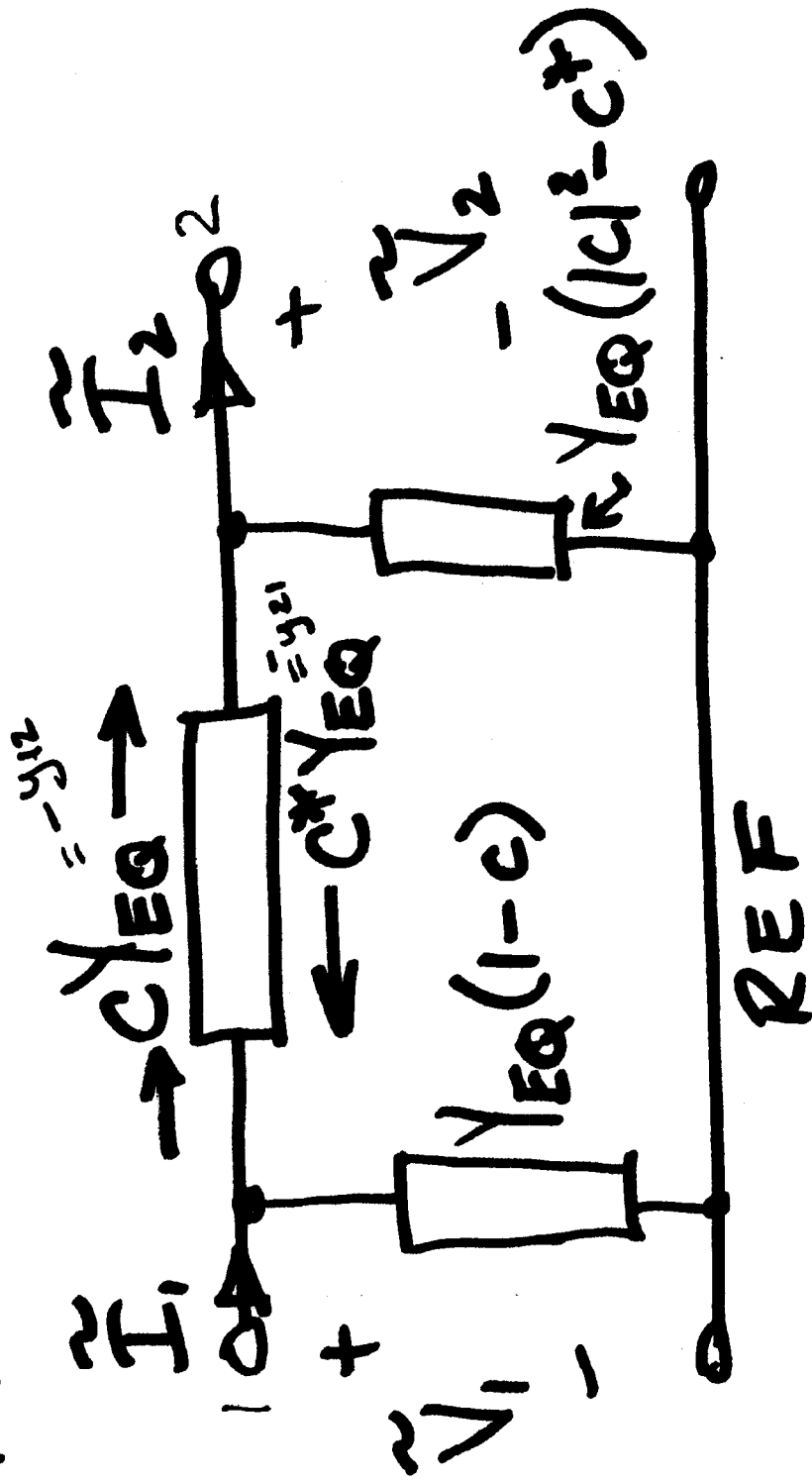$[Y]$ into an equivalent 2-bus network, then



f

Observations:

- LTC (TCL) has a C that is Real.

\therefore Transfer Admittances

$$C Y_{EQ} = C^* Y_{EQ} \\ \Rightarrow \text{Bilateral. } (y_{12} = y_{21})$$

- Phase-Shifter (PS) has complex C .

\therefore Transfer admittances

$$C Y_{EQ} \neq C^* Y_{EQ}$$

$$y_{12} \neq y_{21}$$

Not Bilateral.

$[Y]$ not symm.
(about main diag.)