

EE 582 - LECTURE 4

Mar 15, 2000

Reminder - Friday Homework

3.2

3.3

3.4



3.6

3.12

Next Topic: Cap Bank Switching
Print out paper
for Friday's Lecture!

Today: - RLC Circuits
- Practical Approach
- ATP Simulations
(10am Thurs - Edison)

PARALLEL RLC - SERIES RLC ²

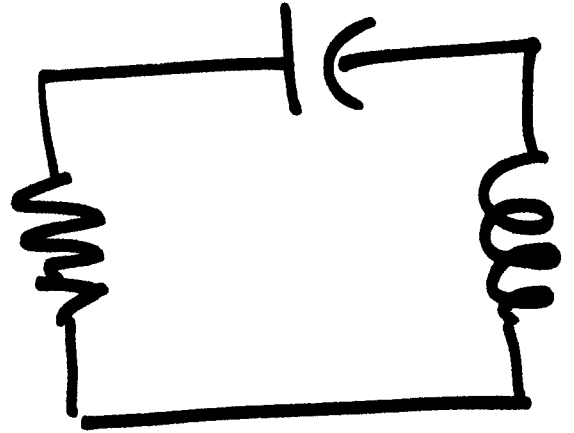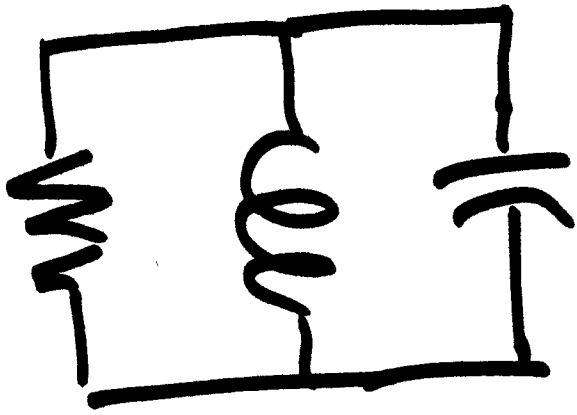

Resonant freq:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Exponential Damping Coefficient
(or Neper freq)

$$\alpha = \frac{1}{2RC}$$

$$\alpha = \frac{R}{2L}$$

Damped or "Natural" Resonant freq

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Damping:

3

Critical Damping: $\alpha = \omega_0$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 0$$

Overdamped:

$$\alpha > \omega_0$$

Underdamped:

$$\omega_0 > \alpha$$


Undamped: $\alpha = 0$

$$\omega_d = \omega_0$$



Look at series RLC

4

SER. RLC. adp

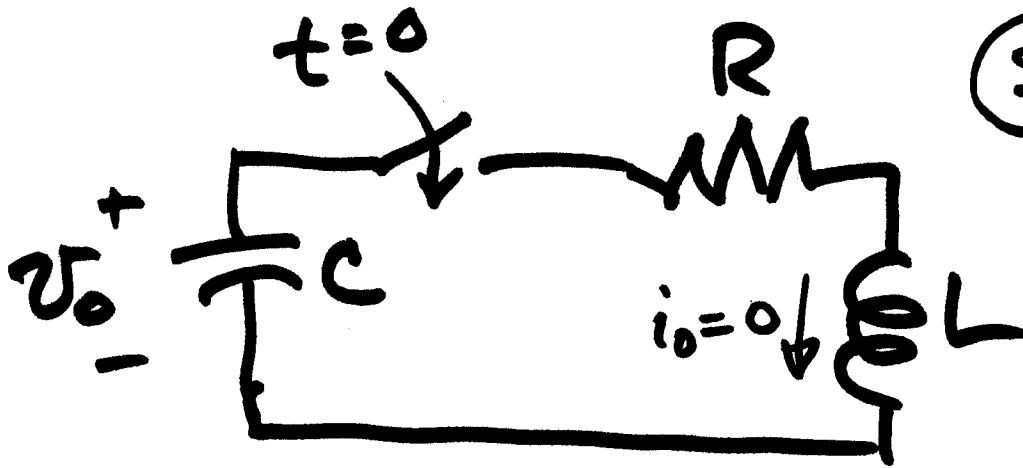

UNDAMPED $R = 0$

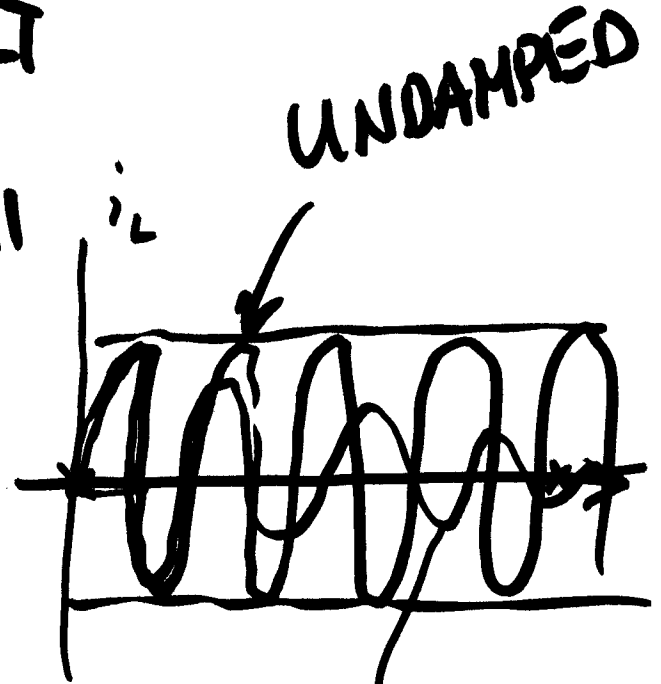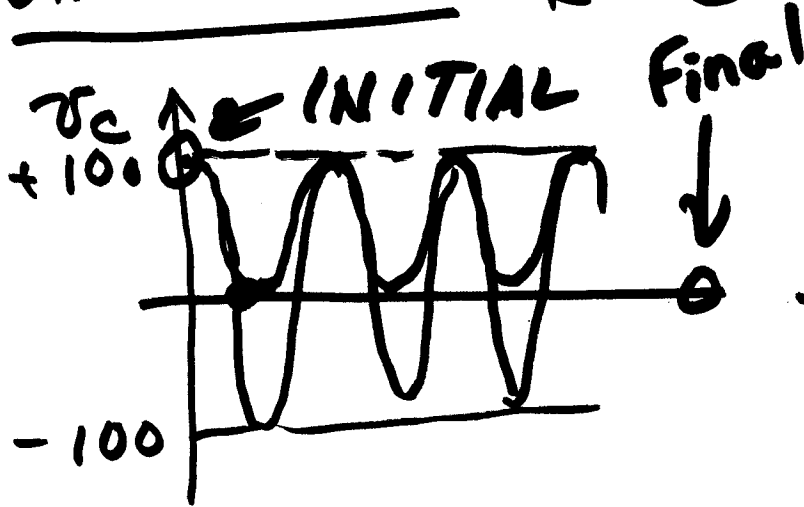

DAMPED

Ex: $L = 10 \text{ mH}$
 $C = 1 \mu\text{F}$
 $R \approx 0$

② $\omega_0 = 10,000 \text{ s}^{-1}$
 $f = \approx 1591 \text{ Hz}$
 $T = 0.63 \text{ ms}$
 $\Delta t \approx 20 \mu\text{s}$
 $T_{\text{END}} =$

① $Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{.01}{10^{-6}}} = 100 \Omega$

$I_p = \frac{\Delta V}{Z_0}$

Read Ch. 4 - § 4.3 - Damping⁵

Make transition from

$$\alpha, \omega_0, \omega_d$$

to $\boxed{s = \sigma + j\omega}$

~~int~~ in terms of Z_0, R, τ, π

More on simulation:

Critically damped:

$$\alpha = \omega_0 = \frac{R}{2L}$$

Check: decrease R

$$\alpha = 10,000 = \frac{R}{(2)(.01)}$$

$$\Rightarrow \underline{R = 200 \Omega}$$


$$R = 190 \Omega \Rightarrow \alpha = \frac{R}{2L}$$
$$= \frac{190}{(2)(1.01)}$$
$$= 9500$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$
$$= \sqrt{10,000^2 - 9500^2} = 3122 \text{ s}^{-1}$$
$$= 497 \text{ Hz}$$
$$T = 2 \text{ ms}$$

$R = 10,000 \rightarrow$ overdamped


Forced RLC Responses

(F_RLC)

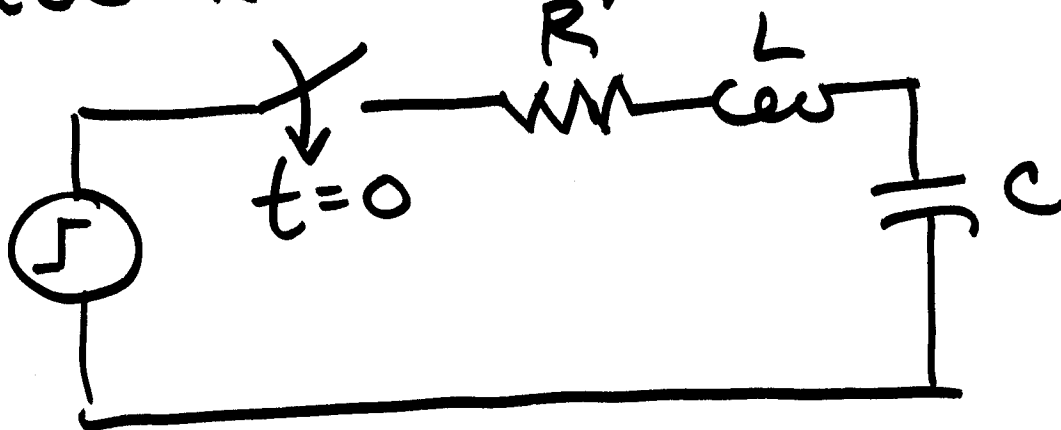

Note: Very similar to

SF_RLC.adp


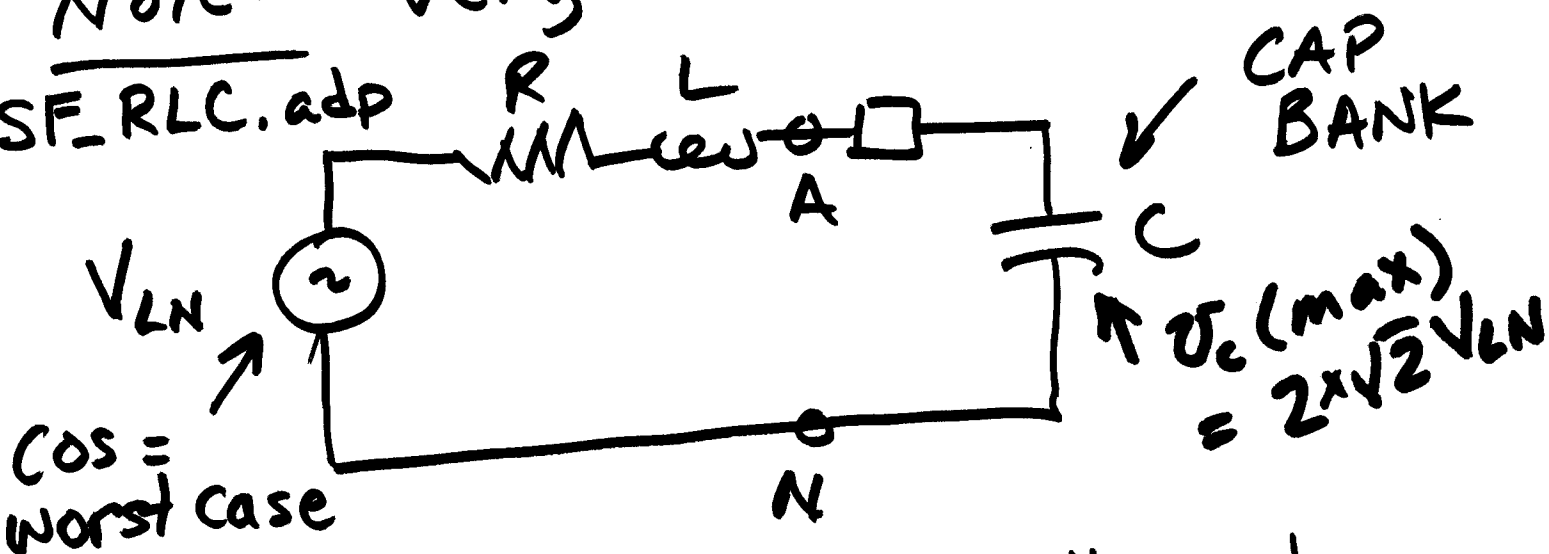


since L is very small and C is sizeable

Then $\omega_0 \gg 377$

Then we can assume that
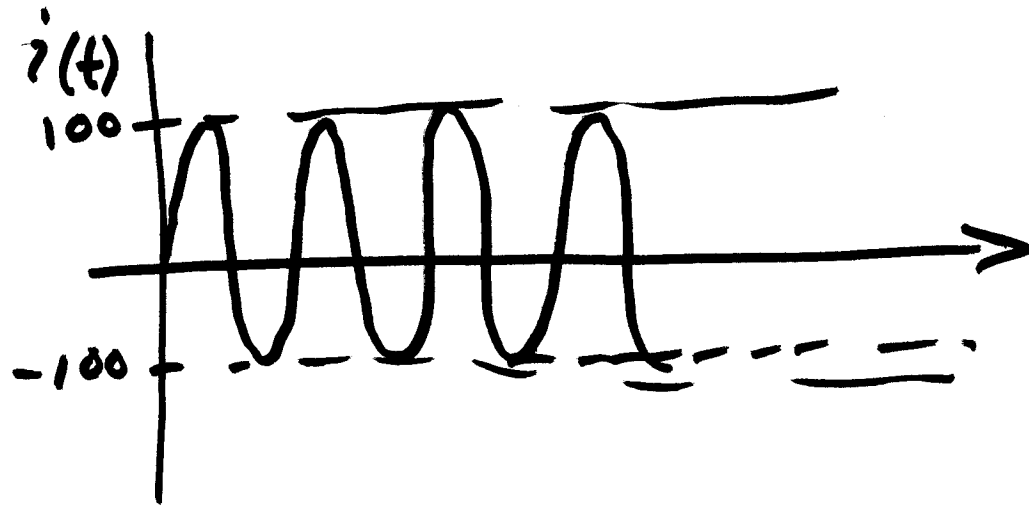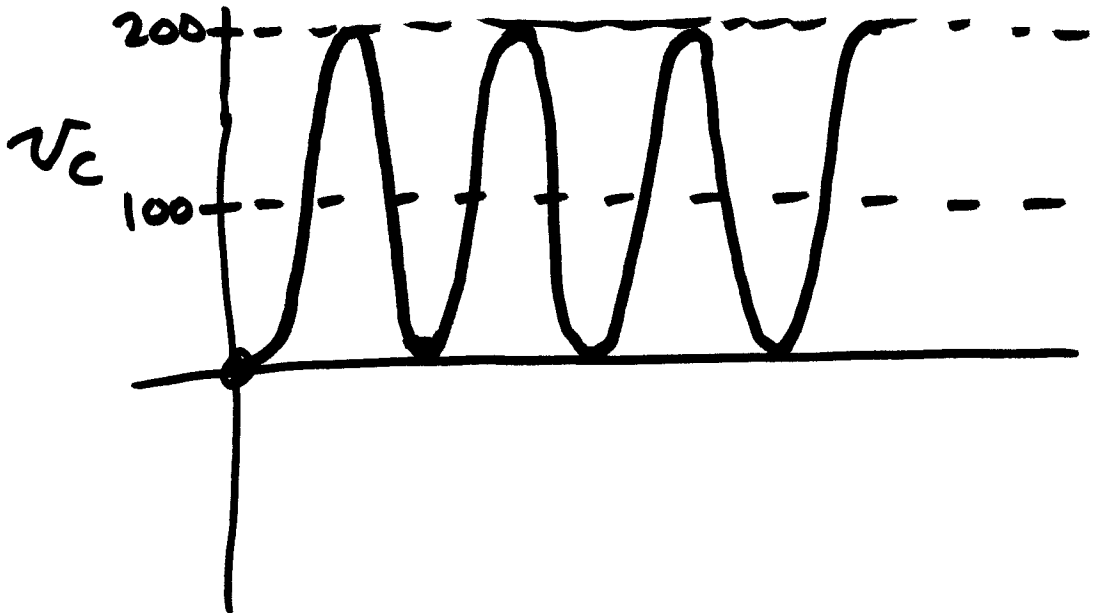
$$V_p \cos 377t \rightleftharpoons V_p \text{ (DC source symbol)}$$



If $\frac{X}{R}$ ratio is 10, then

$$R = \frac{X}{10} = \frac{377L}{10} = \underline{\underline{0.377\Omega}}$$